


Fuente Vpulse

V1


V1 = 0
V2 = 3V
TD = 50n
TR = 10n
TF = 10n
PW = 10n
PER = 1



Forma de onda

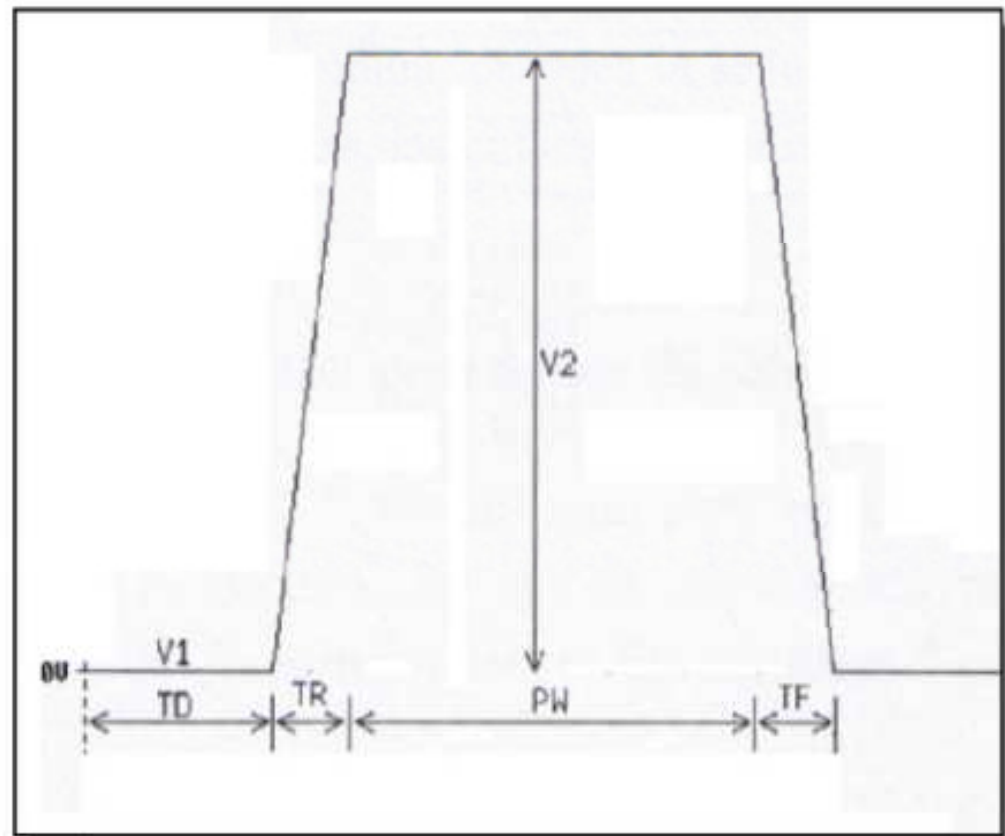

Circuito de medida

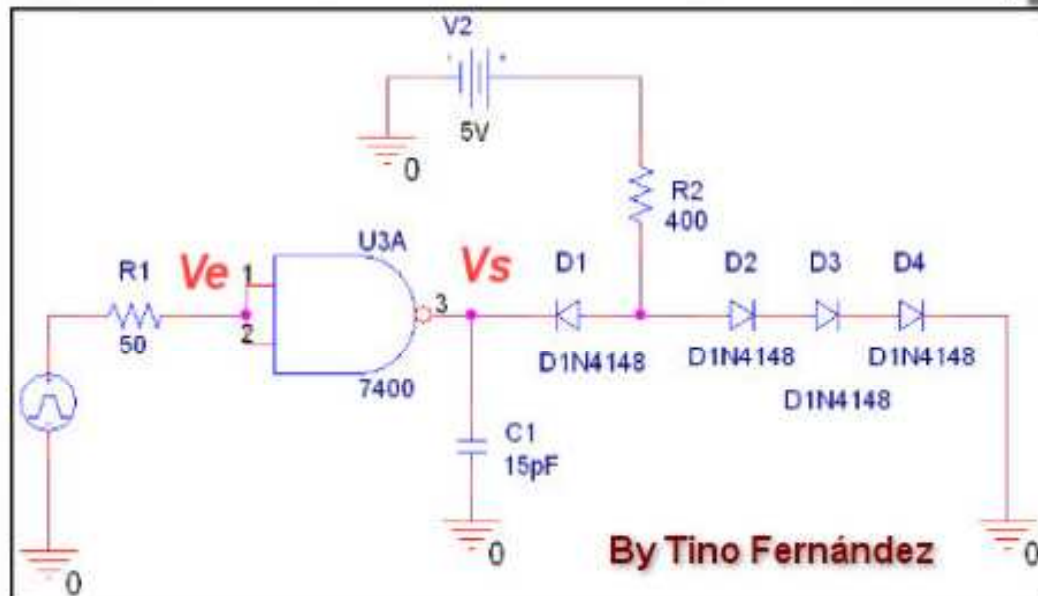

Tiempos de retardo

